

Assignment 3

Preliminaries

1. You can reuse and build upon your previous code for this assignment.
2. We provide you with the following additional functions that help to handle BJT elements.
 - a) `npnBJT.m` is function that adds the element BJT to the list of the BJTs. It serves a similar functionality as the `diode.m` function.
 - b) `fvect.m` is the function that adds the nonlinear stamp to the vector $\mathbf{F}(\mathbf{X})$. You can use this function to fill the $\mathbf{F}(\mathbf{X})$ vector.
 - b. `nljacobian.m` is the function that creates/ updates the Jacobian for the nonlinear elements. Similar, to `diode` add the Jacobian for the BJT in this function.
3. For adding the AC sources to the circuit, use the function named `vol_ac.m`. The `vol_ac.m` function creates a global variable `bac`. The variable `bac` contains the contribution of DC sources.
The addition of DC sources to the circuit can be done using the `vol.m` function.
4. In your submission please provide all code in a zip file in a way that allows us to run the testbenches ourselves (include all code, not just the recent one).
4. Also submit a pdf file containing the answers to the questions, the output plots and the code for functions you have written for this assignment.

Question I

Write a matlab function `dcsolvealpha.m` that finds the dc solution of the augmented system:

$$GX + f(X) = \alpha B_{dc}$$

The functions is defined as follows:

```
function Xdc = dcsolvealpha(Xguess,alpha,maxerr)
% Compute dc solution using newtwn iteration for the augmented system
% G*X + f(X) = alpha*b
% Inputs:
% Xguess is the initial guess for Newton Iteration
% alpha is a paramter (see definition in augmented system above)
% maxerr defined the stopping criterion from newton iteration: Stop the
% iteration when norm(deltaX)<maxerr
% Oupputs:
% Xdc is a vector containing the solution of the augmented system
```

Deliverables:

1. Submit the matlab file `dcsolvealpha.m` containing your function
2. Include the code above in your PDF file submission for the assignment.

Question II

1. Write a matlab function `dcsolvecont.m` that finds the dc solution using the power ramping continuation method. Hint: It may be convenient for you to use the function you developed in Question I. The `dcsolvecont.m` function is defined as follows:

```
function Xdc = dcsolvecont(n_steps,maxerr)
% Compute dc solution using newtwn iteration and continuation method
% (power ramping approach)
% inputs:
% n_steps is the number of continuation steps between zero and one that are
% to be taken. For the purposes of this assignments the steps should be
% linearly spaced (the matlab function "linspace" may be useful).
% maxerr is the stopping criterion for newton iteration (stop iteration
% when norm(deltaX)<maxerr
```

2. Test this function by finding the dc solution (at node V_o) of the following diode circuit at three different values of V_i (-10V, -2V, and 8V). Use 10 continuation steps in this test. Note, we provide the netlist for this circuit in the file `Sedra4_93.m`. All diodes in this circuit have $I_s=2e-15A$ and $V_t=26e-3V$.
3. Run the provided script: `TestBenchDiodeckt4_93.m` shown in Figure 1, This script will use your `dcsolvecont.m` function in order to compute and plot V_o as a function of V_i .

Deliverables

1. The matlab function `dcsolvecont.m`
2. A pdf file containing the matlab function `dcsolvecont.m`. The solutions found in part 2, and the plot provided by the script in part

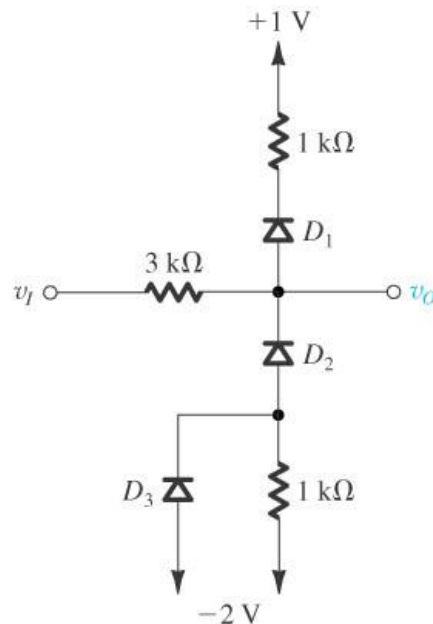


Figure 1: Diode circuit.

Question III

Using the transistor model shown in Appendix, add the contribution of the BJT in the circuit simulator. Complete the contribution of BJT in MATLAB functions named *f_vect.m* and *nlJacobian.m*.

Deliverables:

After completing the stamp of the BJT in circuit simulator. Run the file named *BJT_CB.m* containing the circuit shown below in Figure 2.

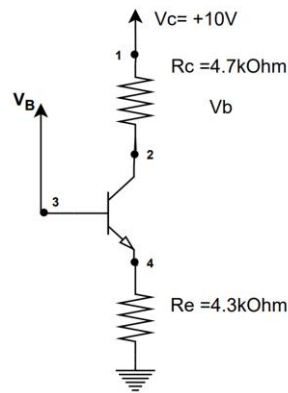


Figure 2: BJT circuit.

Compute the DC solution of the circuit shown in Figure 2 for the following values of base node, $V_B = 4\text{V}$, 6V and 0V .

1. Run the *BJT_CB.m* using the *dcsolve.m* function you implemented in Assignment 1. Report your observations.
2. Run the *BJT_CB.m* using the *dcsolvecont.m* function you implemented in Question II. Report the values of the nodal voltages obtained after using *dcsolvecont.m*.

Question IV

Plot the AC response of the circuit shown in Figure 3 between 0Hz to 5000Hz. Complete the function names *nlACresponse.m* and write your algorithm for computing the AC response. To run the file named *BJT_CE.m* containing the circuit shown below in Figure 3.

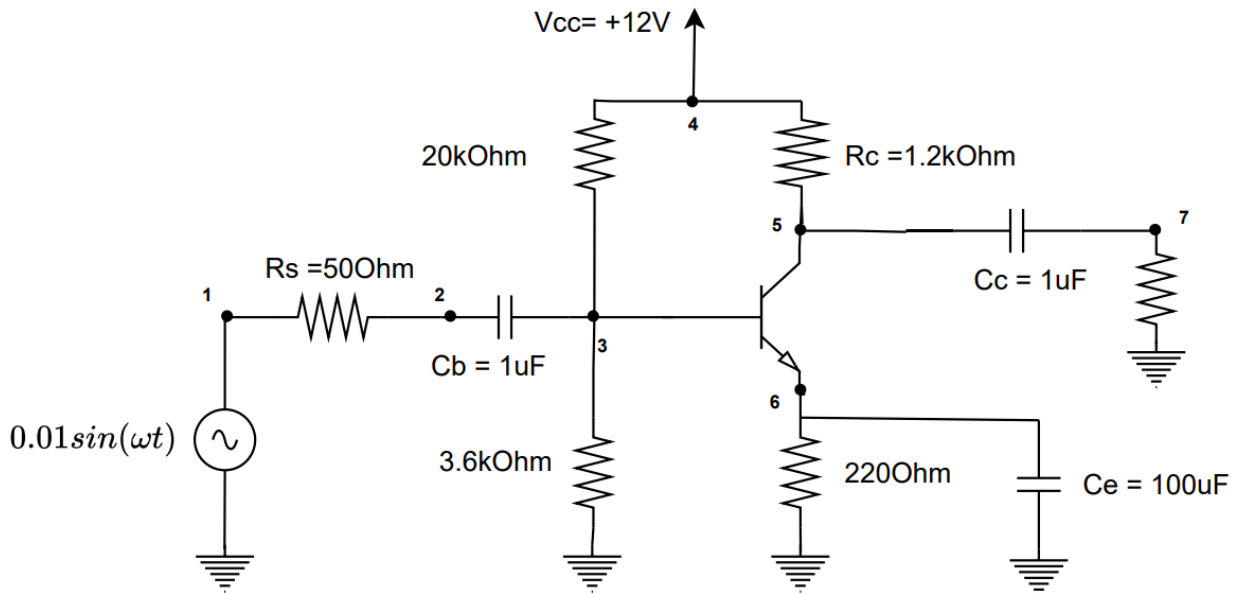


Figure 3: Common Emitter circuit.

1. Run the *BJT_CE.m* and plot the gain at node 7 for the frequencies between 0 to 10^6 Hz obtained and include it in the assignment.

Appendix

Figure 1 below shows the Ebers-Moll model of a NPN BJT transistor. In this assignment you are required to model the BJT using the MNA equations.

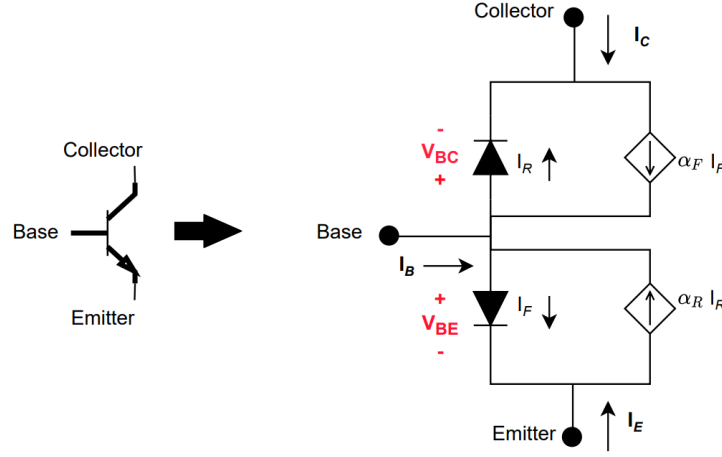


Figure 4: Ebers-Moll model of BJT.

The currents I_F and I_R , are the currents in the Base-Emitter and Base-Collector Junction, respectively. The equations of junction currents I_F and I_R are shown below in (1.1) and (1.2), respectively.

$$I_F = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad (1.1)$$

$$I_R = I_S \left(e^{\frac{V_{BC}}{V_T}} - 1 \right) \quad (1.2)$$

V_{BE} is voltage difference between base and emitter nodes. V_{BC} is voltage difference between base and collector nodes. I_S and V_T are the saturation current and thermal voltages for the Base-Emitter and Base-Collector Junctions. α_F and α_R are forward and reverse coefficients.

The using the Ebers-Moll model for I_E , emitter current, and I_C , collector current, are obtained as shown in (1.3) and (1.4)

$$I_E = -I_F + \alpha_R I_R \quad (1.3)$$

$$I_C = -I_R + \alpha_F I_F \quad (1.4)$$

Using the Kirchhoff's Law, we can obtain the equation for base current

$$I_B = -(I_E + I_C) \quad (1.5)$$

$$I_B = I_F - \alpha_F I_F + I_R - \alpha_R I_R \quad (1.6)$$

These are the nonlinear equations of currents and can be stamped in the MNA equation as shown in (1.7)

$$\underbrace{\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}}_{\mathbf{G}} \underbrace{\begin{bmatrix} V_C \\ V_B \\ V_E \end{bmatrix}}_{\mathbf{X}} + \underbrace{\begin{bmatrix} -I_R + \alpha_F I_F \\ I_F - \alpha_F I_F + I_R - \alpha_R I_R \\ -I_F + \alpha_R I_R \end{bmatrix}}_{\mathbf{F}(\mathbf{X})} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{B}} \quad (1.7)$$

As can be in seen in (1.7), only nonlinear vector $\mathbf{F}(\mathbf{X})$ contains the contribution of the BJT.